

INDEX

Topic	page number
1. Problem Statement,Abstract	01
2. Algorithm and design entity	02
3. Basic Building Blocks	03
Full adder	
11-bit ripple carry adder	
8-bit ripple carry adder	
64-bit ripple carry adder	
Mux	
D-Flipflop	
65-bit register	
4. Architecture	24
5. Controller	28
6. Vhdl code for Floating point multiplier	37

PROBLEM STATEMENT:

Design and develop structural VHDL mode for 32-bit Floating Point Shift and Add Multiplier using Top-Down approach ,Simulate to verify the functionality and analyse the performance metrics.

ABSTRACT:

Floating point multiplication is a crucial operation in high power computing applications . In this project Multiplier is designed in VHDL environment and simulation results are obtained by Xiling's tool. IEEE 754 support different floating point formats such as Single Precision format, Double Precision format, Quadruple Precision format etc.

 



Fig. 1 Floating point formats in the proposed model

Fig. 1 shows the different IEEE 754 floating point formats used commonly. The Single precision format is of 32-bit wide and Double precision format is of 64-bit wide. The Most Significant Bit is the sign bit. The exponent is a signed integer. It is often represented as an unsigned value by adding a bias. In Single precision format, the exponent is of 8-bit wide and the bias is 127, i.e. the exponent has a range of -127 to 128. In Double precision format, the exponent is of 11-bit wide and the bias is 1023, i.e. the exponent has a range of -1023 to 1024. The mantissa or significant of Single precision format is of 23-bit and of double precision format is of 52 bit wide.

ALGORITHM:


Shift and multiplication:

 This algorithm is same as the method we use to multiply two numbers on pen and paper .



To obtain the exponent of the resultant product simply add the exponents of two numbers and check if the position of the most significant 1 of the product is sum of exponent of two numbers plus 1, if that is not the case then find the no. of digits in between these two bits (the most significant one and the sum of exponents) and add that number to the exponent . Since the first digit represents the sign , the sign of the resultant operation can be obtained by XOR operation on the sign bits.

DESIGN ENTITY:

 

BUILDING BLOCKS:

FULL ADDER:

Design entity:



VHDL CODE FOR FULL ADDER:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity fa is
```

```
    Port ( a : in STD_LOGIC;
```

```
          b : in STD_LOGIC;
```

```
          cin : in STD_LOGIC;
```

```
          sum : out STD_LOGIC;
```

```
          cout : out STD_LOGIC);
```

```
end fa;
```

```
architecture Behavioral of fa is
```

```
begin
```


```
    sum <= a xor b xor cin;
```

```
    cout <= (a and b) or (b and cin) or (cin and a);
```

```
end Behavioral;
```

11-BIT RIPPLE CARRY ADDER:

Design entity:

 

VHDL CODE FOR 11-BIT RIPPLE CARRY ADDER:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity rca11 is
```

```
    Port ( a : in STD_LOGIC_VECTOR (10 downto 0);
```

```
          b : in STD_LOGIC_VECTOR (10 downto 0);
```

```
          cin : in STD_LOGIC;
```

```
          cout : out STD_LOGIC;
```

```
          sum : out STD_LOGIC_VECTOR (10 downto 0));
```

```
end rca11;
```

```
architecture Behavioral of rca11 is
```

```
    component fa
```

```
        Port ( a : in STD_LOGIC;
```

```
              b : in STD_LOGIC;
```

```
              cin : in STD_LOGIC;
```

```
              sum : out STD_LOGIC;
```

```
              cout : out STD_LOGIC);
```

```
end component;

signal c1,c2,c3,c4,c5,c6,c7,c8,c9,c10:std_logic;

begin

b1: fa port map(a(0),b(0),cin,sum(0),c1);

b2: fa port map(a(1),b(1),c1,sum(1),c2);

b3: fa port map(a(2),b(2),c2,sum(2),c3);

b4: fa port map(a(3),b(3),c3,sum(3),c4);

b5: fa port map(a(4),b(4),c4,sum(4),c5);

b6: fa port map(a(5),b(5),c5,sum(5),c6);

b7: fa port map(a(6),b(6),c6,sum(6),c7);

b8: fa port map(a(7),b(7),c7,sum(7),c8);


b9: fa port map(a(8),b(8),c8,sum(8),c9);

b10: fa port map(a(9),b(9),c9,sum(9),c10);


b11: fa port map(a(10),b(10),c10,sum(10),cout);

end Behavioral;
```

RTL Schematic:

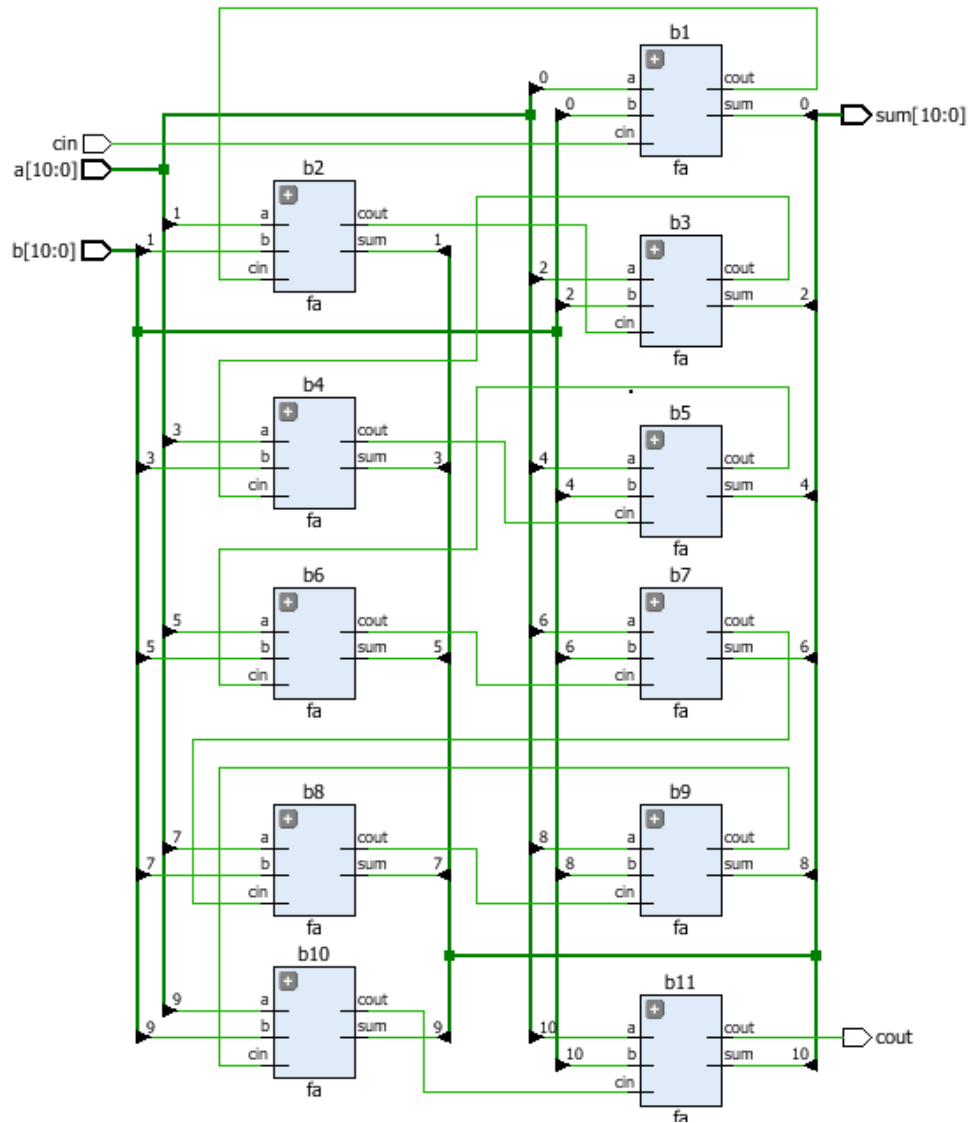


simulation results:

 

8-BIT RIPPLE CARRY ADDER:

Design entity:

 

vhdl code for 8-bit ripple carry adder:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity rca8 is
```

```
    Port ( x : in STD_LOGIC_VECTOR (7 downto 0);
```

```
          y : in STD_LOGIC_VECTOR (7 downto 0);
```

```
          cin : in STD_LOGIC;
```

```
          cout : out STD_LOGIC;
```

```
          z : out STD_LOGIC_VECTOR (7 downto 0));
```

```
end rca8;
```

```
architecture Behavioral of rca8 is
```

```
    component fa
```

```
        Port ( a : in STD_LOGIC;
```

```
              b : in STD_LOGIC;
```

```
              cin : in STD_LOGIC;
```

```
              sum : out STD_LOGIC;
```



```
        cout : out STD_LOGIC);

end component;


signal c1,c2,c3,c4,c5,c6,c7:std_logic;

begin

f1: fa port map(x(0),y(0),cin,z(0),c1);
f2: fa port map(x(1),y(1),c1,z(1),c2);
f3: fa port map(x(2),y(2),c2,z(2),c3);
f4: fa port map(x(3),y(3),c3,z(3),c4);
f5: fa port map(x(4),y(4),c4,z(4),c5);
f6: fa port map(x(5),y(5),c5,z(5),c6);
f7: fa port map(x(6),y(6),c6,z(6),c7);
f8: fa port map(x(7),y(7),c7,z(7),cout);


end Behavioral;
```

RTL Schematic:

 

64-BIT RIPPLE CARRY ADDER:

design entity:

 

VHDL CODE FOR 64-BIT RIPPLE CARRY ADDER:

library IEEE;

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity rca64 is
```

```
    Port ( a : in STD_LOGIC_VECTOR (63 downto 0);
```

```
          b : in STD_LOGIC_VECTOR (63 downto 0);
```

```
          cin : in STD_LOGIC;
```

```
          cout : out STD_LOGIC;
```

```
          sum : out STD_LOGIC_VECTOR (63 downto 0));
```

```
end rca64;
```

```
architecture Behavioral of rca64 is
```

```
    component rca8
```

```
        Port ( x : in STD_LOGIC_VECTOR (7 downto 0);
```

```
              y : in STD_LOGIC_VECTOR (7 downto 0);
```

```
              cin : in STD_LOGIC;
```

```
              cout : out STD_LOGIC;
```

```
              z : out STD_LOGIC_VECTOR (7 downto 0));
```

```
    end component;
```

```
    signal c1,c2,c3,c4,c5,c6,c7:std_logic;
```

```
    begin
```

```
        a1: rca8 port map(a(7 downto 0),b(7 downto 0),cin,c1,sum(7 downto 0));
```

```
        a2: rca8 port map(a(15 downto 8),b(15 downto 8),c1,c2,sum(15 downto 8));
```


```
        a3: rca8 port map(a(23 downto 16),b(23 downto 16),c2,c3,sum(23 downto 16));
```

```
        a4: rca8 port map(a(31 downto 24),b(31 downto 24),c3,c4,sum(31 downto 24));
```

```
        a5: rca8 port map(a(39 downto 32),b(39 downto 32),c4,c5,sum(39 downto 32));
```


```
        a6: rca8 port map(a(47 downto 40),b(47 downto 40),c5,c6,sum(47 downto 40));
```
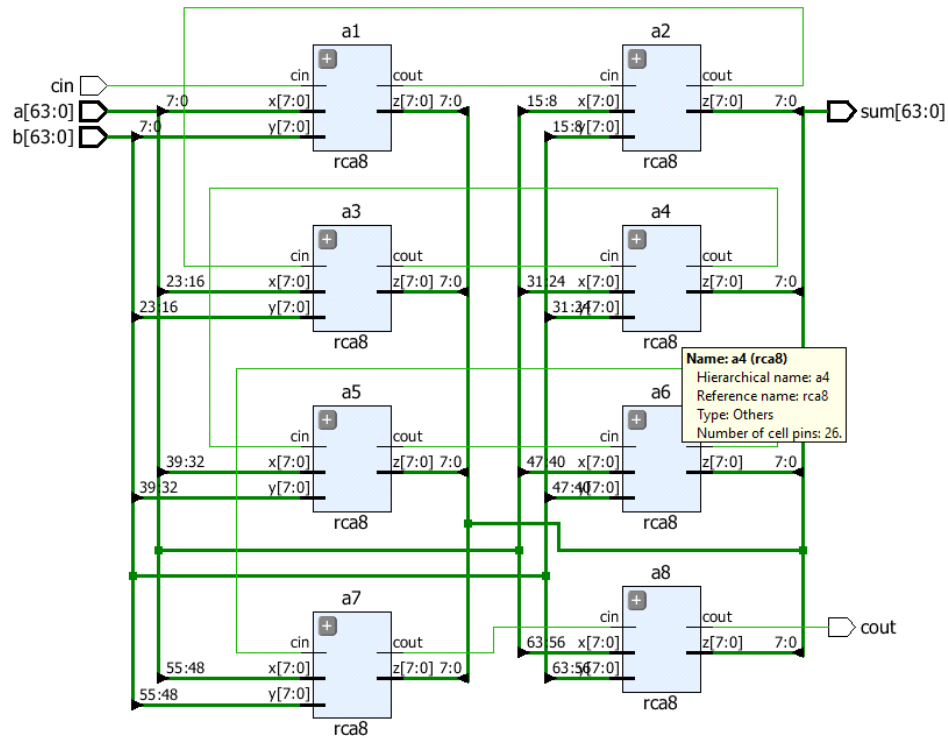
```
        a7: rca8 port map(a(55 downto 48),b(55 downto 48),c6,c7,sum(55 downto 48));
```



MUX

Design entity:

 

vhdl code for mux:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity mux is
```

```
    Port ( a : in STD_LOGIC;
```

```
          b : in STD_LOGIC;
```

```
          c : in STD_LOGIC;
```

```
          d : in STD_LOGIC;
```

```
          e1 : in STD_LOGIC;
```

```
          s0 : in STD_LOGIC;
```

```
          s1 : in STD_LOGIC;
```

```
          s2 : in STD_LOGIC;
```

```
          y : out STD_LOGIC);
```

```
end mux;
```

```
architecture Behavioral of mux is
```

```
begin
```

```
    process(s0,s1,s2,a,b,c,d,e1)
```

```

begin

if (s0='0' and s1='0' and s2='0') then y<=a;

elseif(s0='0' and s1='0' and s2='1') then y<=b;

elseif (s0='0' and s1='1' and s2='0') then y<=c;

elseif (s0='0' and s1='1' and s2='1') then y<=d;

else y<=e1;

end if;


end process;

end Behavioral;

```

D-FLIPFLOP:

design entity:

 

vhdl code for d-flipflop:

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity dff is

    Port ( d : in STD_LOGIC;

          clk : in STD_LOGIC;

          q : out STD_LOGIC);

end dff;

```

architecture Behavioral of dff is

begin

process(clk)

begin

if (clk='1' and clk'event) then q<=d ;


end if;

end process;

end Behavioral;

64-BIT REGISTER:

design entity:

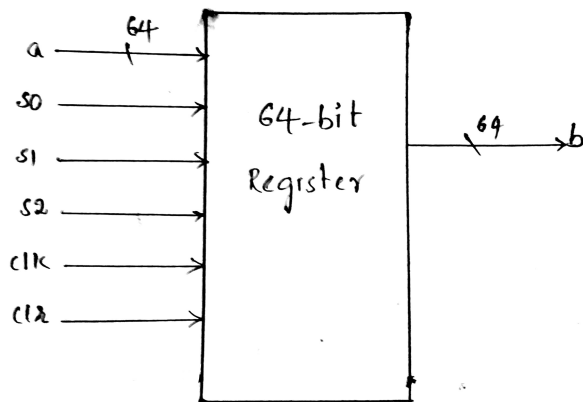

VHDL CODE FOR 64 BIT REGISTER:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity usr64 is

Port (a : in STD_LOGIC_VECTOR (63 downto 0);

b : out STD_LOGIC_VECTOR (63 downto 0);

s0 : in STD_LOGIC;

```
s1 : in STD_LOGIC;  
s2 : in STD_LOGIC;  
clk : in STD_LOGIC;  
clr : in STD_LOGIC);
```

```
end usr64;
```

architecture Behavioral of usr64 is

component dff

```
Port ( d : in STD_LOGIC;  
      clk : in STD_LOGIC;  
      q : out STD_LOGIC);
```

```
end component;
```

component mux

```
Port ( a : in STD_LOGIC;  
      b : in STD_LOGIC;  
      c : in STD_LOGIC;  
      d : in STD_LOGIC;  
      e1 : in STD_LOGIC;  
      s0 : in STD_LOGIC;  
      s1 : in STD_LOGIC;  
      s2 : in STD_LOGIC;  
      y : out STD_LOGIC);
```

```
end component;
```

signal

```
m1,m2,m3,m4,m5,m6,m7,m8,m9,m10,m11,m12,m13,m14,m15,m16,m17,m18,m19,m20,m21,  
m22,m23,m24,m25,m26,m27,m28,m29,m30,m31,m32,m33,m34,m35,m36,m37,m38,m39,m40  
,m41,m42,m43,m44,m45,m46,m47,m48,m49,m50,  
m51,m52,m53,m54,m55,m56,m57,m58,m59,m60,
```


m61,m62,m63,m64,q1,q2,q3,q4,q5,q6,q7,q8,q9,q10,q11,q12,q13,q14,q15,q16,q17,q18,q19,q20,q21,q22,q23,q24,q25,q26,q27,q28,q29,q30,q31,q32,q33,q34,q35,q36,q37,q38,q39,q40,q41,q42,q43,q44,q45,q46,q47,q48,q49,q50,q51,q52,q53,q54,q55,q56,q57,q58,q59,q60,q61,q62,q63,q64:std_logic;

begin

mu1: mux port map(clr,a(0),clr,q2,q1,s0,s1,s2,m1);

mu2: mux port map(clr,a(1),q1,q3,q2,s0,s1,s2,m2);

mu3: mux port map(clr,a(2),q2,q4,q3,s0,s1,s2,m3);

mu4: mux port map(clr,a(3),q3,q5,q4,s0,s1,s2,m4);

mu5: mux port map(clr,a(4),q4,q6,q5,s0,s1,s2,m5);

mu6: mux port map(clr,a(5),q5,q7,q6,s0,s1,s2,m6);

mu7: mux port map(clr,a(6),q6,q8,q7,s0,s1,s2,m7);

mu8: mux port map(clr,a(7),q7,q9,q8,s0,s1,s2,m8);

mu9: mux port map(clr,a(8),q8,q10,q9,s0,s1,s2,m9);

mu10: mux port map(clr,a(9),q9,q11,q10,s0,s1,s2,m10);

mu11: mux port map(clr,a(10),q10,q12,q11,s0,s1,s2,m11);

mu12: mux port map(clr,a(11),q11,q13,q12,s0,s1,s2,m12);

mu13: mux port map(clr,a(12),q12,q14,q13,s0,s1,s2,m13);

mu14: mux port map(clr,a(13),q13,q15,q14,s0,s1,s2,m14);

mu15: mux port map(clr,a(14),q14,q16,q15,s0,s1,s2,m15);

mu16: mux port map(clr,a(15),q15,q17,q16,s0,s1,s2,m16);

mu17: mux port map(clr,a(16),q16,q18,q17,s0,s1,s2,m17);

mu18: mux port map(clr,a(17),q17,q19,q18,s0,s1,s2,m18);

mu19: mux port map(clr,a(18),q18,q20,q19,s0,s1,s2,m19);

mu20: mux port map(clr,a(19),q19,q21,q20,s0,s1,s2,m20);

mu21: mux port map(clr,a(20),q20,q22,q21,s0,s1,s2,m21);

mu22: mux port map(clr,a(21),q21,q23,q22,s0,s1,s2,m22);

mu23: mux port map(clr,a(22),q22,q24,q23,s0,s1,s2,m23);
mu24: mux port map(clr,a(23),q23,q25,q24,s0,s1,s2,m24);
mu25: mux port map(clr,a(24),q24,q26,q25,s0,s1,s2,m25);
mu26: mux port map(clr,a(25),q25,q27,q26,s0,s1,s2,m26);
mu27: mux port map(clr,a(26),q26,q28,q27,s0,s1,s2,m27);
mu28: mux port map(clr,a(27),q27,q29,q28,s0,s1,s2,m28);
mu29: mux port map(clr,a(28),q28,q30,q29,s0,s1,s2,m29);
mu30: mux port map(clr,a(29),q29,q31,q30,s0,s1,s2,m30);
mu31: mux port map(clr,a(30),q30,q32,q31,s0,s1,s2,m31);
mu32: mux port map(clr,a(31),q31,q33,q32,s0,s1,s2,m32);
mu33: mux port map(clr,a(32),q32,q34,q33,s0,s1,s2,m33);
mu34: mux port map(clr,a(33),q33,q35,q34,s0,s1,s2,m34);
mu35: mux port map(clr,a(34),q34,q36,q35,s0,s1,s2,m35);
mu36: mux port map(clr,a(35),q35,q37,q36,s0,s1,s2,m36);
mu37: mux port map(clr,a(36),q36,q38,q37,s0,s1,s2,m37);
mu38: mux port map(clr,a(37),q37,q39,q38,s0,s1,s2,m38);
mu39: mux port map(clr,a(38),q38,q40,q39,s0,s1,s2,m39);
mu40: mux port map(clr,a(39),q39,q41,q40,s0,s1,s2,m40);
mu41: mux port map(clr,a(40),q40,q42,q41,s0,s1,s2,m41);
mu42: mux port map(clr,a(41),q41,q43,q42,s0,s1,s2,m42);
mu43: mux port map(clr,a(42),q42,q44,q43,s0,s1,s2,m43);
mu44: mux port map(clr,a(43),q43,q45,q44,s0,s1,s2,m44);
mu45: mux port map(clr,a(44),q44,q46,q45,s0,s1,s2,m45);
mu46: mux port map(clr,a(45),q45,q47,q46,s0,s1,s2,m46);
mu47: mux port map(clr,a(46),q46,q48,q47,s0,s1,s2,m47);

```
mu48: mux port map(clr,a(47),q47,q49,q48,s0,s1,s2,m48);
mu49: mux port map(clr,a(48),q48,q50,q49,s0,s1,s2,m49);
mu50: mux port map(clr,a(49),q49,q51,q50,s0,s1,s2,m50);
mu51: mux port map(clr,a(50),q50,q52,q51,s0,s1,s2,m51);
mu52: mux port map(clr,a(51),q51,q53,q52,s0,s1,s2,m52);
mu53: mux port map(clr,a(52),q52,q54,q53,s0,s1,s2,m53);
mu54: mux port map(clr,a(53),q53,q55,q54,s0,s1,s2,m54);
mu55: mux port map(clr,a(54),q54,q56,q55,s0,s1,s2,m55);
mu56: mux port map(clr,a(55),q55,q57,q56,s0,s1,s2,m56);
mu57: mux port map(clr,a(56),q56,q58,q57,s0,s1,s2,m57);
mu58: mux port map(clr,a(57),q57,q59,q58,s0,s1,s2,m58);
mu59: mux port map(clr,a(58),q58,q60,q59,s0,s1,s2,m59);
mu60: mux port map(clr,a(59),q59,q61,q60,s0,s1,s2,m60);
mu61: mux port map(clr,a(60),q60,q62,q61,s0,s1,s2,m61);
mu62: mux port map(clr,a(61),q61,q63,q62,s0,s1,s2,m62);
mu63: mux port map(clr,a(62),q62,q64,q63,s0,s1,s2,m63);
mu64: mux port map(clr,a(63),q63,clr,q64,s0,s1,s2,m64);

d1: dff port map(m1,clk,q1);
d2: dff port map(m2,clk,q2);
d3: dff port map(m3,clk,q3);
d4: dff port map(m4,clk,q4);
d5: dff port map(m5,clk,q5);
d6: dff port map(m6,clk,q6);
d7: dff port map(m7,clk,q7);
d8: dff port map(m8,clk,q8);
```

d9: dff port map(m9,clk,q9);
d10: dff port map(m10,clk,q10);
d11: dff port map(m11,clk,q11);
d12: dff port map(m12,clk,q12);
d13: dff port map(m13,clk,q13);
d14: dff port map(m14,clk,q14);
d15: dff port map(m15,clk,q15);
d16: dff port map(m16,clk,q16);
d17: dff port map(m17,clk,q17);
d18: dff port map(m18,clk,q18);
d19: dff port map(m19,clk,q19);
d20: dff port map(m20,clk,q20);
d21: dff port map(m21,clk,q21);
d22: dff port map(m22,clk,q22);
d23: dff port map(m23,clk,q23);
d24: dff port map(m24,clk,q24);
d25: dff port map(m25,clk,q25);
d26: dff port map(m26,clk,q26);
d27: dff port map(m27,clk,q27);
d28: dff port map(m28,clk,q28);
d29: dff port map(m29,clk,q29);
d30: dff port map(m30,clk,q30);
d31: dff port map(m31,clk,q31);
d32: dff port map(m32,clk,q32);
d33: dff port map(m33,clk,q33);

d34: dff port map(m34,clk,q34);
d35: dff port map(m35,clk,q35);
d36: dff port map(m36,clk,q36);
d37: dff port map(m37,clk,q37);
d38: dff port map(m38,clk,q38);
d39: dff port map(m39,clk,q39);
d40: dff port map(m40,clk,q40);
d41: dff port map(m41,clk,q41);
d42: dff port map(m42,clk,q42);
d43: dff port map(m43,clk,q43);
d44: dff port map(m44,clk,q44);
d45: dff port map(m45,clk,q45);
d46: dff port map(m46,clk,q46);
d47: dff port map(m47,clk,q47);
d48: dff port map(m48,clk,q48);
d49: dff port map(m49,clk,q49);
d50: dff port map(m50,clk,q50);
d51: dff port map(m51,clk,q51);
d52: dff port map(m52,clk,q52);
d53: dff port map(m53,clk,q53);
d54: dff port map(m54,clk,q54);
d55: dff port map(m55,clk,q55);
d56: dff port map(m56,clk,q56);
d57: dff port map(m57,clk,q57);
d58: dff port map(m58,clk,q58);

d59: dff port map(m59,clk,q59);

d60: dff port map(m60,clk,q60);

d61: dff port map(m61,clk,q61);

d62: dff port map(m62,clk,q62);

d63: dff port map(m63,clk,q63);

d64: dff port map(m64,clk,q64);

b(0)<=q1;

b(1)<=q2;

b(2)<=q3;

b(3)<=q4;

b(4)<=q5;

b(5)<=q6;

b(6)<=q7;

b(7)<=q8;

b(8)<=q9;

b(9)<=q10;

b(10)<=q11;

b(11)<=q12;

b(12)<=q13;

b(13)<=q14;

b(14)<=q15;

b(15)<=q16;

b(16)<=q17;

b(17)<=q18;

b(18)<=q19;

$b(19) \leq q_{20};$

$b(20) \leq q_{21};$

$b(21) \leq q_{22};$

$b(22) \leq q_{23};$

$b(23) \leq q_{24};$

$b(24) \leq q_{25};$

$b(25) \leq q_{26};$

$b(26) \leq q_{27};$

$b(27) \leq q_{28};$

$b(28) \leq q_{29};$

$b(29) \leq q_{30};$

$b(30) \leq q_{31};$

$b(31) \leq q_{32};$

$b(32) \leq q_{33};$

$b(33) \leq q_{34};$

$b(34) \leq q_{35};$

$b(35) \leq q_{36};$

$b(36) \leq q_{37};$

$b(37) \leq q_{38};$

$b(38) \leq q_{39};$

$b(39) \leq q_{40};$

$b(40) \leq q_{41};$


$b(41) \leq q_{42};$

$b(42) \leq q_{43};$

$b(43) \leq q_{44};$


b(44)<=q45;
b(45)<=q46;
b(46)<=q47;
b(47)<=q48;
b(48)<=q49;
b(49)<=q50;
b(50)<=q51;
b(51)<=q52;
b(52)<=q53;
b(53)<=q54;
b(54)<=q55;
b(55)<=q56;
b(56)<=q57;
b(57)<=q58;
b(58)<=q59;
b(59)<=q60;
b(60)<=q61;
b(61)<=q62;
b(62)<=q63;
b(63)<=q64;
end Behavioral;

simulation results:

 

ARCHITECTURE:

Design entity:

 

Vhdl code for architecture:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity architech is

Port (a : in STD_LOGIC_VECTOR (31 downto 0);

b : in STD_LOGIC_VECTOR (31 downto 0);

c : out STD_LOGIC_VECTOR (63 downto 0);

ac : inout STD_LOGIC_VECTOR (63 downto 0);

u :in std_logic_vector(10 downto 0);

s02 : in STD_LOGIC;

s12 : in STD_LOGIC;

s22 : in STD_LOGIC;

s03 : in STD_LOGIC;

s13 : in STD_LOGIC;

s23 : in STD_LOGIC;

s04 : in STD_LOGIC;

s14 : in STD_LOGIC;

s24 : in STD_LOGIC;

s05 : in STD_LOGIC;

s15 : in STD_LOGIC;

s25 : in STD_LOGIC;

clk : in STD_LOGIC;

clr : in STD_LOGIC;

cin : in std_logic);

end architech;

architecture Behavioral of architech is

component usr64

Port (a : in STD_LOGIC_VECTOR (63 downto 0);


b : out STD_LOGIC_VECTOR (63 downto 0);

s0 : in STD_LOGIC;

s1 : in STD_LOGIC;


s2 : in STD_LOGIC;

[illegible]


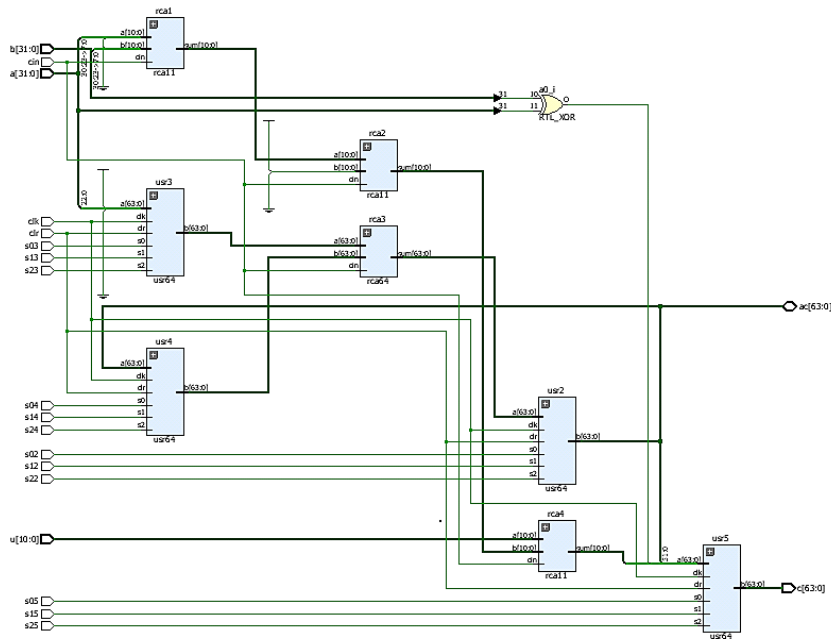


CONTROLLER:

Design entity:

 

design:

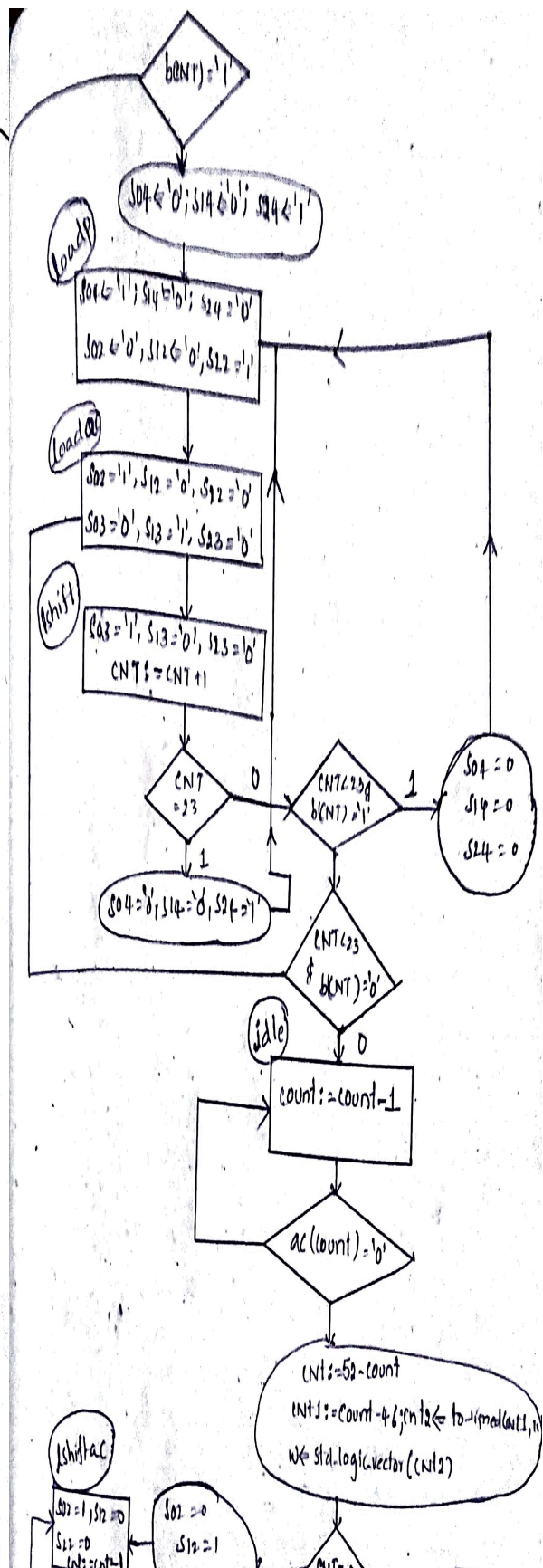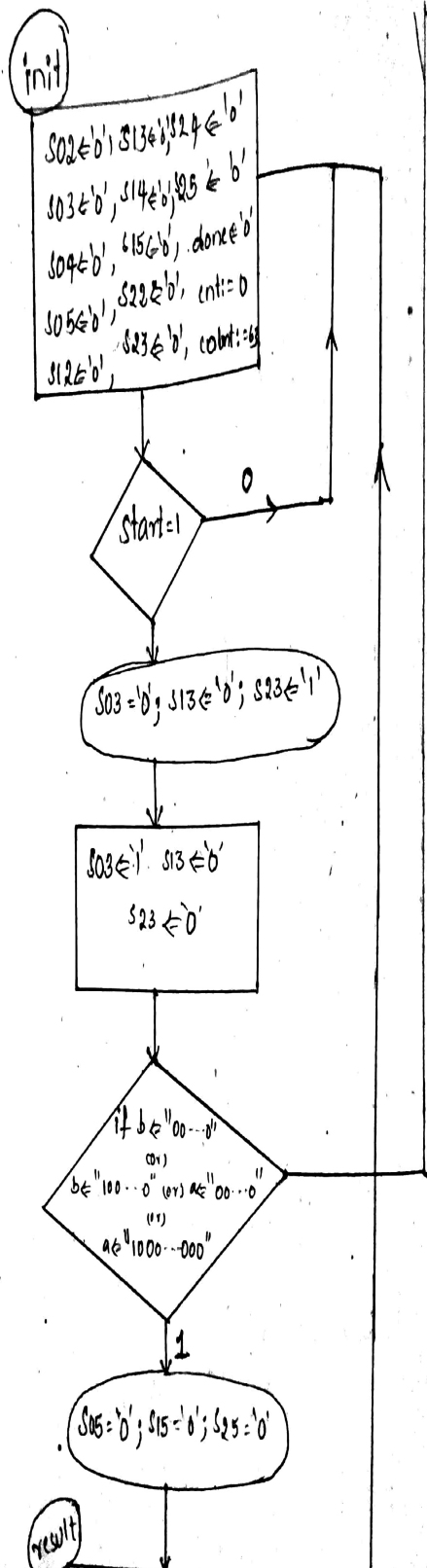

Vhdl code for controller:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;

entity controller is

Port (a : in STD_LOGIC_VECTOR (31 downto 0);

b : in STD_LOGIC_VECTOR (31 downto 0);

ac : in STD_LOGIC_VECTOR (63 downto 0);

clk : in STD_LOGIC;

start : in STD_LOGIC;

w: out std_logic_vector(10 downto 0);

s02 : out STD_LOGIC;

s03 : out STD_LOGIC;

s04 : out STD_LOGIC;

s05 : out STD_LOGIC;

s12 : out STD_LOGIC;

s13 : out STD_LOGIC;

s14 : out STD_LOGIC;

s15 : out STD_LOGIC;

s22 : out STD_LOGIC;

s23 : out STD_LOGIC;

s24 : out STD_LOGIC;

```
s25 : out STD_LOGIC;  
done : out STD_logic);  
end controller;
```

architecture Behavioral of controller is

type state is (init,loadr,loadp,loadac,lshift,lshiftac,idle,loadc,result);

signal ps,ns : state;

shared variable cnt,count,cnt1:integer;

signal cnt2 : signed(10 downto 0);

begin

ns_logic:process(ps,clk)

begin

case ps is

when init=>

s02<='0';

s03<='0';

s04<='0';

s05<='0';

s12<='0';

s13<='0';

s14<='0';

s15<='0';

s22<='0';

s23<='0';

s24<='0';

s25<='0';

cnt:=0;

count:=63;

done<='0';

if start ='1' then

s03<='0';

s13<='0';

s23<='1';

ns<=loadr;

else ns<=init;

end if;

if (clk='1' and clk'event) then

ps<=ns;

end if;

when loadr =>

s03<='1';

s13<='0';

s23<='0';

```
if (b="00000000000000000000000000000000") or  
(b="10000000000000000000000000000000") or (a="00000000000000000000000000000000")  
or (a="10000000000000000000000000000000") then
```

```
    s05<='0';
```

```
    s15<='0';
```

```
    s25<='0';
```

```
    ns<=result;
```

```
elseif b(cnt)='1' then
```

```
    s04<='0';
```

```
    s14<='0';
```

```
    s24<='1';
```

```
    ns<=loadp;
```

```
else ns<=loadac;
```

```
end if;
```

```
if (clk='1' and clk'event) then
```

```
    ps<=ns;
```

```
end if;
```

```
when loadp => s04<='1';
```

```
    s14<='0';
```

```
    s24<='0';
```

```
    s02<='0';
```

```
    s12<='0';
```

```
    s22<='1';
```

```
    ns<=loadac;
```

```
    if (clk='1' and clk'event) then
```

```
        ps<=ns;
```

```

        end if;

when loadac => s02<='1';

    s12<='0';

    s22<='0';

    s03<='0';

    s13<='1';

    s23<='0';

    ns<=lshift;

    if (clk='1' and clk'event) then

        ps<=ns;

        cnt:=cnt+1;

        end if;

when lshift => s03<='1';

    s13<='0';

    s23<='0';

    if cnt=23 then

        s04<='0';

        s14<='0';

        s24<='1';

        ns<=loadp;

    elsif (cnt<23 and b(cnt)='1') then

        s04<='0';

        s14<='0';

        s24<='1';

        ns<=loadp;

```

```

    elsif (cnt<23 and b(cnt)='0') then
        ns<=loadac;

    else

        ns<=idle;

    end if;

    if (clk='1' and clk'event) then

        ps<=ns;

    end if;

when idle => if ac(count)='0' then

    ns<=idle;

    if (clk='1' and clk'event) then

        count := count-1;

        ps<=ns;

    end if;

else

    cnt := 52-count;

    cnt1 := count-46;

    cnt2 <= to_signed(cnt1,11);

    w<= std_logic_vector(cnt2);

    if cnt=0 then

        s05<='0';

        s15<='0';

        s25<='1';

        ns<=loadc;

```

```

        else s02<='0';

            s12<='1';

            s22<='0';

            ns<=lshiftac;

        end if;

    if (clk='1' and clk'event) then

        count := count-1;

        ps<=ns;

    end if;

end if;

when lshiftac => s02<='1';

    s12<='0';

    s22<='0';


    if cnt=1 then

        s05<='0';

        s15<='0';

        s25<='1';

        ns<=loadc;

    else s02<='0';

        s12<='1';

        s22<='0';

        ns<=lshiftac;

    end if;

    if (clk='1' and clk'event) then

```

```

        cnt :=cnt-1;

        ps<=ns;

    end if;

when loadc => done<='1';

    ns<=init;

    if (clk='1' and clk'event) then

        ps<=ns;

    end if;

when result=> done<='1';

    ns<=init;

    if (clk='1' and clk'event) then

        ps<=ns;

    end if;

when others =>

    if (clk='1' and clk'event) then

        ps<=init;

    end if;

end case;

end process;

end Behavioral;

```

VHDL CODE FOR 32-BIT FLOATING POINT MULTIPLIER:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity fpm32 is

Port (a : in STD_LOGIC_VECTOR (31 downto 0);

b : in STD_LOGIC_VECTOR (31 downto 0);

c : out STD_LOGIC_VECTOR (63 downto 0);

start : in STD_LOGIC;

done : out STD_LOGIC;

clk : in STD_LOGIC;

cin : in STD_LOGIC;

clr : in std_logic);

end fpm32;

architecture Behavioral of fpm32 is

component architech

Port (a : in STD_LOGIC_VECTOR (31 downto 0);

b : in STD_LOGIC_VECTOR (31 downto 0);

c : out STD_LOGIC_VECTOR (63 downto 0);

ac : inout STD_LOGIC_VECTOR (63 downto 0);

u :in std_logic_vector(10 downto 0);

s02 : in STD_LOGIC;

s12 : in STD_LOGIC;

s22 : in STD_LOGIC;

s03 : in STD_LOGIC;

s13 : in STD_LOGIC;

s23 : in STD_LOGIC;

s04 : in STD_LOGIC;

s14 : in STD_LOGIC;

s24 : in STD_LOGIC;

s05 : in STD_LOGIC;

s15 : in STD_LOGIC;

s25 : in STD_LOGIC;

clk : in STD_LOGIC;

clr : in STD_LOGIC;

cin : in std_logic);

end component;

component controller

Port (a : in STD_LOGIC_VECTOR (31 downto 0);

b : in STD_LOGIC_VECTOR (31 downto 0);

ac : in STD_LOGIC_VECTOR (63 downto 0);

clk : in STD_LOGIC;

start : in STD_LOGIC;

w: out std_logic_vector(10 downto 0);

s02 : out STD_LOGIC;

s03 : out STD_LOGIC;

s04 : out STD_LOGIC;

s05 : out STD_LOGIC;

s12 : out STD_LOGIC;

s13 : out STD_LOGIC;

s14 : out STD_LOGIC;


```

s15 : out STD_LOGIC;

s22 : out STD_LOGIC;

s23 : out STD_LOGIC;

s24 : out STD_LOGIC;

s25 : out STD_LOGIC;

done : out STD_logic );

end component;

signal s02,s12,s22,s03,s13,s23,s04,s14,s24,s05,s15,s25:std_logic;

signal ac :STD_LOGIC_VECTOR (63 downto 0);

signal w:std_logic_vector(10 downto 0);

begin


arc: architech port map(a,b,c,ac,w,s02,s12,s22,s03,s13,s23,s04,s14,s24,s05,s15,s25,clk,clr,cin);

cont: controller port
map(a,b,ac,clk,start,w,s02,s03,s04,s05,s12,s13,s14,s15,s22,s23,s24,s25,done);

end Behavioral;

```

RTL Schematic:

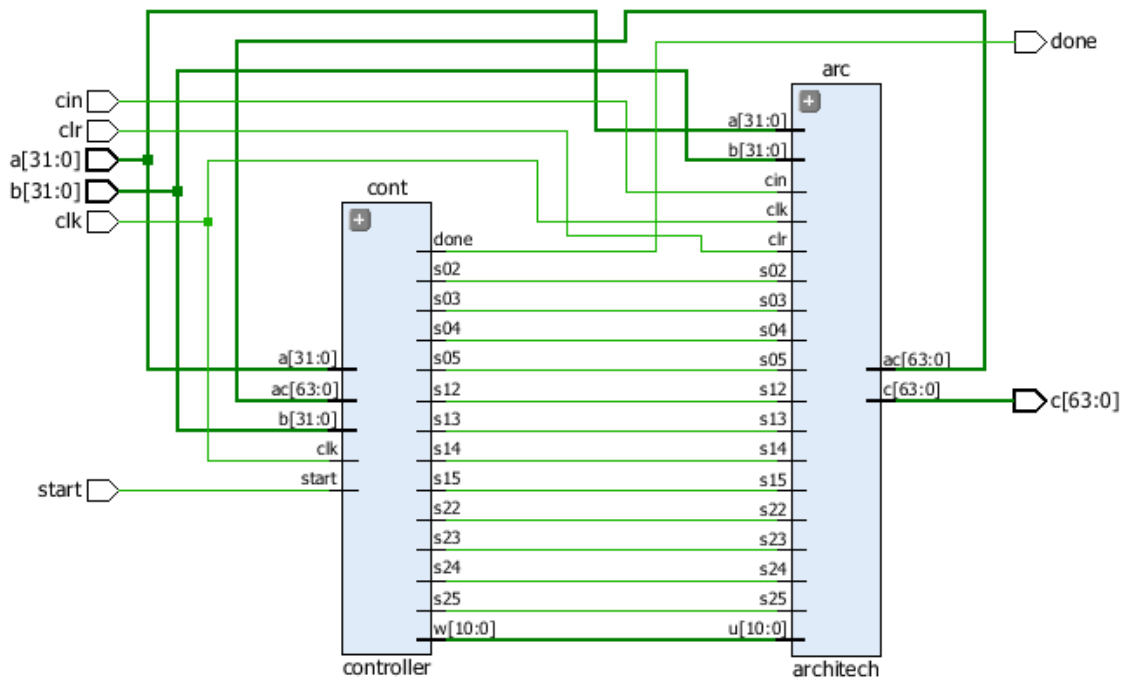

simulation results:

